

COMMUNICATIONS I

SOLUTIONS TO PROBLEM SHEET NINE

1.

$$K_V = \frac{(\tau_L - \tau_0)}{\tau_L + \tau_0} = 0.2$$

$$V_- = K_V V_+ = 0.2V$$

$$I_- = \cancel{0.2V} = -K_V I_+ = -K_V \frac{V_+}{\tau_0} = -4 \text{ mA}$$

$$V_L = (1 + K_V) V_+ = 1.2V$$

$$I_L = (1 - K_V) I_+ = 16 \text{ mA}$$

IF WE ADD A RESISTOR AT THE JUNCTION,
THE NEW LOAD SEEN BY THE 50Ω LINE

IS $R \cdot \tau_L / (R + \tau_L)$. WE WANT THIS NEW

LOAD TO BE EQUAL TO 50Ω (MATCHED
LINES). THEREFORE $R = 150\Omega$.

2.

$$(a) \quad Z_0 = 50 \Omega$$

$$u = 2 \cdot 10^8 \text{ m/SEC}$$

$$(b) \quad Z_{IN} = Z_0 \left[\frac{Z_L + j Z_0 \tan \beta L}{Z_0 + j Z_L \tan \beta L} \right]$$

$$\text{LINE 1} \quad Z_L = +\infty$$

$$\text{THUS} \quad Z_{IN} = \frac{Z_0}{j \tan \beta L}$$

$$\text{LINE 2} \quad Z_L = 0$$

$$\text{THUS} \quad Z_{IN} = j Z_0 \tan \beta L$$

COMBINING IN SERIES

$$Z_{ab} = Z_0 \left(\frac{1}{j \tan \beta L} + j \tan \beta L \right) + Z_0 = 50 \Omega$$

$$\Rightarrow j Z_0 \left(\tan \beta L - \frac{1}{\tan \beta L} \right) = 0$$

$$\Rightarrow \tan \beta L = \frac{1}{\tan \beta L} = 1 \quad \Rightarrow \beta L = \pi/4$$

THUS

$$L = \frac{\pi}{4K} = \frac{\pi}{4} \cdot \frac{2 \cdot 10^8}{2\pi \cdot 10^6} = 25 \text{ m}$$