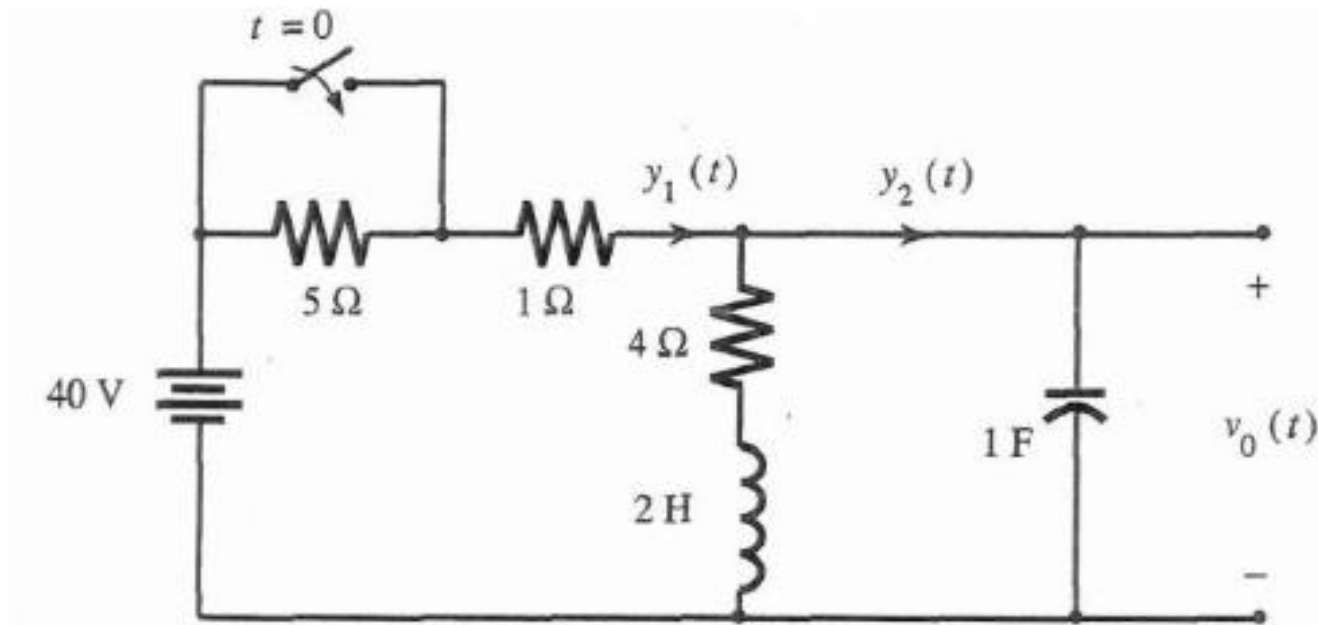


Problem Sheet 5 Question 4

- Problem:** For the circuit shown in the figure below, the switch is in open position for a long time before $t = 0$, when it is closed instantaneously.



Problem Sheet 5 Question 4

a) Let us examine what happens for $t < 0$.

We know that $i_C(t) = C \frac{dv_C(t)}{dt}$ (or $v_C(t) = \frac{1}{C} \int_{-\infty}^t i_C(\tau) d\tau$) and $v_L(t) = L \frac{di_L(t)}{dt}$.


- If the system is in steady state, the current $y_2(t)$ across the capacitor is 0 since the voltage across the capacitor is constant. Therefore, $y_2(0^-) = 0 A$.
- Furthermore, the current $y_1(t)$ which flows through the left loop (Loop 1) is constant and therefore, the voltage across the inductor is 0.
- Based on the above two points, the voltage across the capacitor $v_0(t)$ is the same as the voltage across the 4Ω resistor, i.e., $y_1(t) \cdot 4 V$.

In that case for the left loop (Loop 1) we have:

$$y_1(t) \cdot (5 + 1 + 4) = 40V \Rightarrow y_1(t) = 4 A, t < 0$$

$$v_0(t) = y_1(t) \cdot 4 V = 16V, t < 0$$

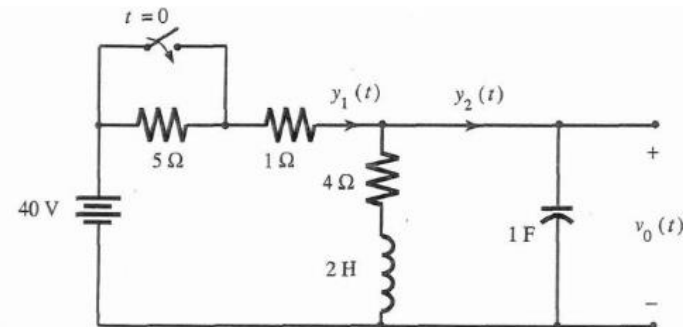Initial conditions: $y_1(0^-) = 4 A, y_2(0^-) = 0 A, v_0(0^-) = 16 V$



Problem Sheet 5 Question 4 cont.

a) Write loop equations in time domain for $t \geq 0$.

Loop 1:

$$L \frac{di_L(t)}{dt} + 4 \cdot i_L(t) + 1 \cdot y_1(t) = 40 u(t)$$


$$i_L(t) = y_1(t) - y_2(t)$$

$$L \left(\frac{dy_1(t)}{dt} - \frac{dy_2(t)}{dt} \right) + 4(y_1(t) - y_2(t)) + 1 \cdot y_1(t) = 40 u(t)$$

$$2 \frac{dy_1(t)}{dt} - 2 \frac{dy_2(t)}{dt} + 5y_1(t) - 4y_2(t) = 40u(t)$$

Loop 2:
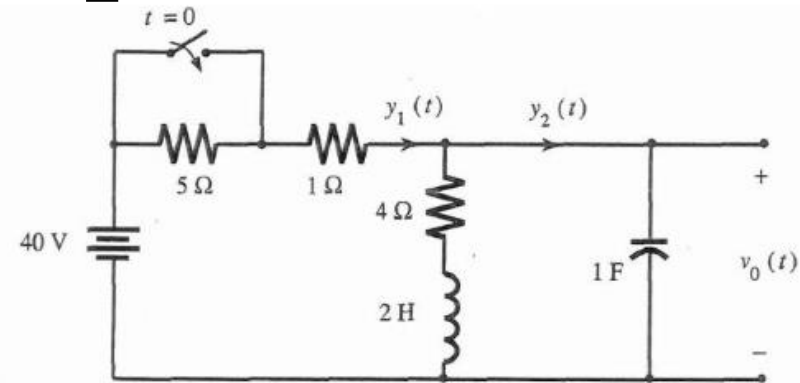
$$L \left(\frac{dy_1(t)}{dt} - \frac{dy_2(t)}{dt} \right) + 4(y_1(t) - y_2(t)) = \frac{1}{C} \int_{-\infty}^t i_C(\tau) d\tau = \frac{1}{C} \int_{-\infty}^t y_2(\tau) d\tau$$



Problem Sheet 5 Question 4 cont.

b) Loop 1 equation in time and Laplace domain for $t \geq 0$.

Loop 1:

$$2 \frac{dy_1(t)}{dt} - 2 \frac{dy_2(t)}{dt} + 5y_1(t) - 4y_2(t) = 40 u(t)$$

$$y_1(0^-) = 4 A$$

$$y_2(0^-) = 0 A$$

$$2[sY_1(s) - y_1(0^-)] - 2[sY_2(s) - y_2(0^-)] + 5Y_1(s) - 4Y_2(s) = 40/s \Rightarrow$$

$$(2s + 5)Y_1(s) - (2s + 4) Y_2(s) = 8 + 40/s$$

Problem Sheet 5 Question 4 cont.

b) Loop 2 equation in time and Laplace domain for $t \geq 0$.

Loop 2:

$$L\left(\frac{dy_1(t)}{dt} - \frac{dy_2(t)}{dt}\right) + 4(y_1(t) - y_2(t)) = \int_{-\infty}^t y_2(\tau) d\tau$$

$$y_1(0^-) = 4 \text{ A}$$

$$y_2(0^-) = 0 \text{ A}$$

$$v_0(0^-) = 16 \text{ V}$$

$$\int_{-\infty}^t x(\tau) d\tau \Leftrightarrow \frac{X(s)}{s} + \frac{1}{s} \int_{-\infty}^{0^-} x(t) dt$$

$$\mathcal{L}\left\{\int_{-\infty}^t y_2(\tau) d\tau\right\} = \frac{Y_2(s)}{s} + \frac{1}{s} \frac{1}{C} \int_{-\infty}^{0^-} y_2(t) dt = \frac{Y_2(s)}{s} + \frac{1}{s} v_0(0^-)$$

$$2[sY_1(s) - y_1(0^-)] - 2[sY_2(s) - y_2(0^-)] + 4Y_1(s) - 4Y_2(s) = \frac{Y_2(s)}{s} + \frac{16}{s}$$

$$-(2s + 4)Y_1(s) + (2s + 4 + \frac{1}{s})Y_2(s) = -8 - \frac{16}{s}$$

Problem Sheet 5 Question 4 cont.

b) Merge equations for Loops 1 and 2 in a matrix form $t \geq 0$

$$\begin{bmatrix} 2s + 5 & -(2s + 4) \\ -(2s + 4) & 2s + 4 + \frac{1}{s} \end{bmatrix} \begin{bmatrix} Y_1(s) \\ Y_2(s) \end{bmatrix} = \begin{bmatrix} 8 + \frac{40}{s} \\ -8 - \frac{16}{s} \end{bmatrix}$$

By solving the above system we obtain:

$$Y_1(s) = \frac{4(6s^2 + 13s + 5)}{s(s^2 + 3s + 2.5)} = \frac{8}{s} + \frac{16s + 28}{(s^2 + 3s + 2.5)}$$

$$Y_2(s) = \frac{20(s + 2)}{(s^2 + 3s + 2.5)}$$

Problem Sheet 5 Question 4 cont.

b) Find $y_1(t)$, $t \geq 0$

$$Y_1(s) = \frac{4(6s^2+13s+5)}{s(s^2+3s+2.5)} = \frac{8}{s} + \frac{16s+28}{s^2+3s+2.5}$$

We use Property 10c from Laplace Properties tables.

$$re^{-at} \cos(bt + \theta) u(t) \Leftrightarrow \frac{As + B}{s^2 + 2as + c}$$

$$r = \sqrt{\frac{A^2c + B^2 - 2ABa}{c - a^2}}$$

$$\theta = \tan^{-1} \left(\frac{Aa - B}{A\sqrt{c - a^2}} \right)$$

$$b = \sqrt{c - a^2}$$

$$A = 16, B = 28, a = 1.5, c = 2.5$$

$$y_1(t) = [8 + 17.89e^{-1.5t} \cos(0.5t - 26.56^\circ)] u(t)$$

Problem Sheet 5 Question 4 cont.

b) Find $y_1(t)$, $t \geq 0$

$$Y_2(s) = \frac{20(s+2)}{(s^2+3s+2.5)} = \frac{20s+40}{(s^2+3s+2.5)}$$

Property 10c

$$r e^{-at} \cos(bt + \theta) u(t) \Leftrightarrow \frac{As + B}{s^2 + 2as + c}$$

$$r = \sqrt{\frac{A^2c + B^2 - 2ABa}{c - a^2}}$$

$$\theta = \tan^{-1} \left(\frac{Aa - B}{A\sqrt{c - a^2}} \right)$$

$$b = \sqrt{c - a^2}$$

$$A = 20, B = 40, a = 1.5, c = 2.5$$

$$y_2(t) = 20\sqrt{2}e^{-1.5t} \cos(0.5t - 45^\circ) u(t)$$